

Lab #2 The only time you have to do math

Hardware/Software Design of Embedded Systems

Iftidar Miah

7 March 2019

1. Purpose

Create a single bit full adder component implemented to create a 4-bit ripple-carry adder. Design an Arithmetic Logic Unit (ALU) that will perform addition, subtraction, increments, decrements, negation, greater than logic, sll, srl, sra, logical nots, ands, ors, xors, xnors, nands, and nors. Implement the ALU design on the Zybo board with buttons, switches, clock, and LEDs.

2. Prelab

i. Theory

Single-bit full adder logic equations for sum and carryout are given by

$$S = (A \text{ XOR } B) \text{ XOR } C_{\text{IN}} = A \oplus B \oplus C$$

$$C_{\text{OUT}} = ((A \text{ XOR } B) \text{ AND } C) \text{ OR } (A \text{ AND } B) = (A \oplus B) C + AB$$


ii. Truth Table

Single bit full adder


A	B	C _{IN}	(A \oplus B)	S = (A \oplus B) \oplus C	(A \oplus B) C	AB	C _{OUT} = (A \oplus B) C + AB
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	1	0	1	0	1
1	0	0	1	1	0	0	0
1	0	1	1	0	1	0	1
1	1	0	0	0	0	1	1
1	1	1	0	1	0	1	1

iii. Schematic

Single Bit Full Adder Black Box

 

4-Bit Ripple Carry Adder Block Diagram

 

3. Part 1

a. Theory

A single bit adder will add 3 bits (A , B , C_{in}) and output S and C_{out} . The logic functions for both are given by the following logic functions and behaves according to the truth table below.

$$S = (A \text{ XOR } B) \text{ XOR } C_{IN} = A \oplus B \oplus C$$

$$C_{OUT} = ((A \text{ XOR } B) \text{ AND } C) \text{ OR } (A \text{ AND } B) = (A \oplus B) C + AB$$


Using a structural model, we can create 4 instances of adder and chain them together to make a ripple carry adder that adds two 4 bit numbers and a single-bit carry in. The end result is a single bit carry out and 4-bit sum that successfully adds 4-bit numbers with a carry in.

b. Truth Table

For a single bit adder

A	B	C_{IN}	S = (A \oplus B) \oplus C	C_{OUT} = (A \oplus B) C + AB
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

c. Schematic

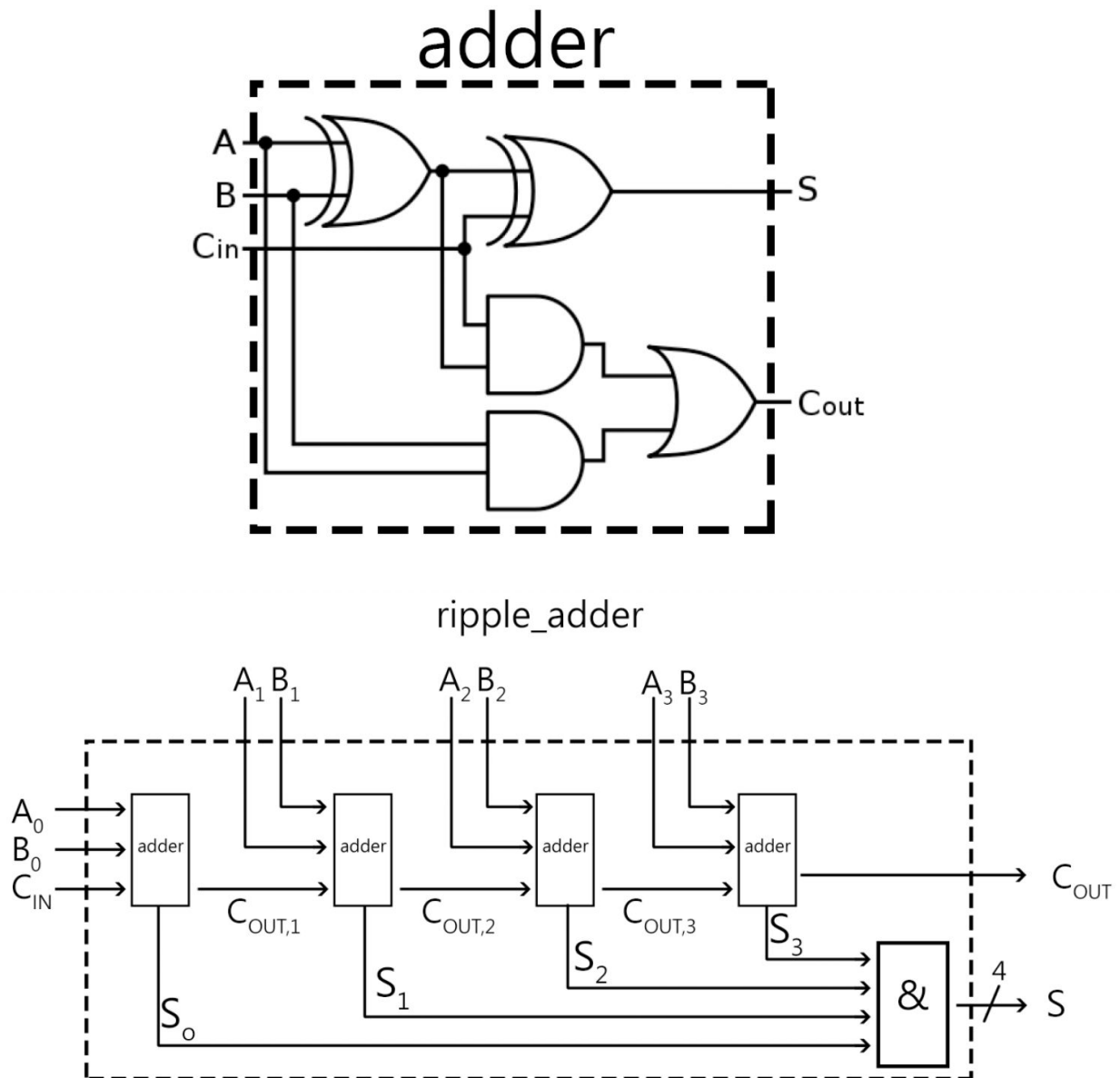

d. Design

Adder.vhd (single bit full adder)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity adder is
    port( A, B, C_in : in  std_logic;
          S, C_out  : out std_logic);
end adder;

architecture adder_arch of adder is

```

```

begin
    S <= (A XOR B) XOR C_in;
    C_out <= ((A XOR B) AND C_in) OR (A AND B);
end adder_arch;

```

ripple_adder.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity ripple_adder is
    port( C_in  : in std_logic;
          A, B  : in std_logic_vector(3 downto 0);
          C_out : out std_logic;
          S     : out std_logic_vector(3 downto 0));
end ripple_adder;

architecture ripple_adder_arch of ripple_adder is
    signal C  : std_logic_vector(2 downto 0); -- Carry ins/outs inside black box

    component adder
        port( A, B, C_in : in  std_logic;
              S, C_out  : out std_logic);
    end component;

begin

    ADD0: adder
        Port Map( A => A(0),
                  B => B(0),
                  C_in => C_in,
                  S => S(0),
                  C_out => C(0)
                );

    ADD1: adder
        Port Map( A => A(1),
                  B => B(1),
                  C_in => C(0),
                  S => S(1),
                  C_out => C(1)
                );

    ADD2: adder
        Port Map( A => A(2),
                  B => B(2),
                  C_in => C(1),
                  S => S(2),
                  C_out => C(2)
                );

    ADD3: adder

```

```

Port Map( A => A(3),
          B => B(3),
          C_in => C(2),
          S => S(3),
          C_out => C_out
);

```

```

end ripple_adder_arch;

```

e. Test

Adder_tb.vhd (for single bit full adder)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std;

entity adder_tb is
end adder_tb;

architecture adder_arch_tb of adder_tb is
    signal A_tb, B_tb, C_in_tb : std_logic := '0'; -- Input test bench signal declarations
    signal S_tb, C_out_tb      : std_logic; -- Output test bench signal declarations

    component adder
        port( A, B, C_in : in std_logic;
              S, C_out  : out std_logic);
    end component;

begin
    A_proc: process
    begin
        wait for 100ns;
        A_tb <= '1';
        wait for 100ns;
        A_tb <= '0';
    end process A_proc;

    B_proc: process
    begin
        wait for 50ns;
        B_tb <= '1';
        wait for 50ns;
        B_tb <= '0';
    end process B_proc;

    C_in_proc: process
    begin
        wait for 25ns;
        C_in_tb <= '1';
        wait for 25ns;
        C_in_tb <= '0';
    end process C_in_proc;

```

```

DUT: adder
  Port Map( A => A_tb,
            B => B_tb,
            C_in => C_in_tb,
            S => S_tb,
            C_out => C_out_tb
          );

end adder_arch_tb;

```



Simulation for single bit adder matches truth table from prelab for a single adder.

Ripple_adder_tb.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity ripple_adder_tb is
end ripple_adder_tb;

architecture ripple_adder_arch_tb of ripple_adder_tb is
  signal C_in_tb : std_logic;
  signal A_tb, B_tb : std_logic_vector(3 downto 0);
  signal C_out_tb : std_logic;
  signal S_tb : std_logic_vector(3 downto 0);

  component ripple_adder
    port( C_in : in std_logic;
          A, B : in std_logic_vector(3 downto 0);
          C_out : out std_logic;
          S : out std_logic_vector(3 downto 0));
  end component;

begin

  A_proc: process
  begin
    wait for 8ns;
    A_tb <= "0000";
    wait for 8ns;
    A_tb <= "0110";
    wait for 8ns;
    A_tb <= "1001";
    wait for 8ns;
    A_tb <= "1111";
  end process A_proc;

```

```


B_proc: process
begin
    wait for 8ns;
    B_tb <= "0000";
    wait for 8ns;
    B_tb <= "1001";
    wait for 8ns;
    B_tb <= "0111";
    wait for 8ns;
    B_tb <= "1001";
end process B_proc;

C_in_proc: process
begin
    wait for 8ns;
    C_in_tb <= '1';
    wait for 8ns;
    C_in_tb <= '0';
    wait for 8ns;
    C_in_tb <= '1';
    wait for 8ns;
    C_in_tb <= '1';
end process C_in_proc;

DUT: ripple_adder
    Port Map( C_in => C_in_tb,
              A => A_tb,
              B => B_tb,
              C_out => C_out_tb,
              S => S_tb
            );

end ripple_adder_arch_tb;

```

 

Simulation for ripple adder shows 4 simple additions.

$$0000 + 0000 + 1 = 0001, C_{OUT} = 0$$



$$0110 + 1001 + 0 = 1111, C_{OUT} = 0$$

$$1001 + 0111 + 1 = 0001, C_{OUT} = 1$$



$$1111 + 1001 + 1 = 1001, C_{OUT} = 1$$


f. Implementation

Single Bit Full Adder

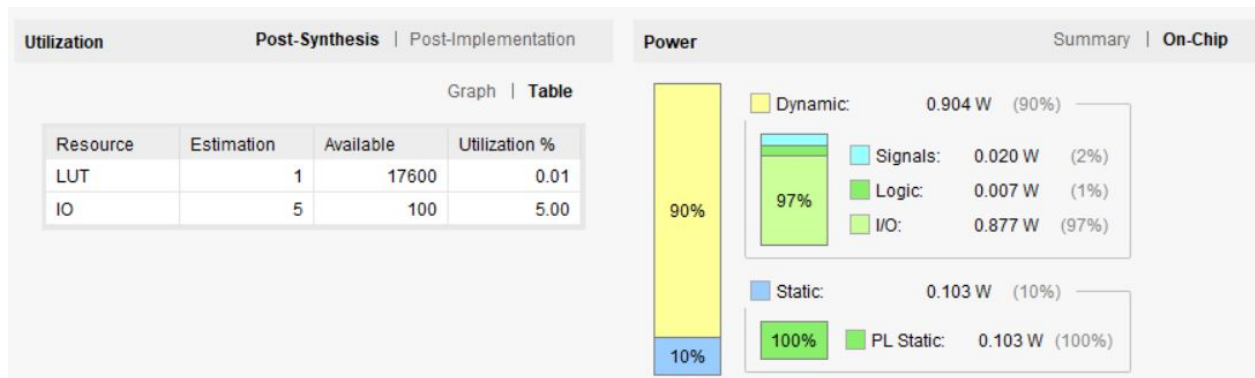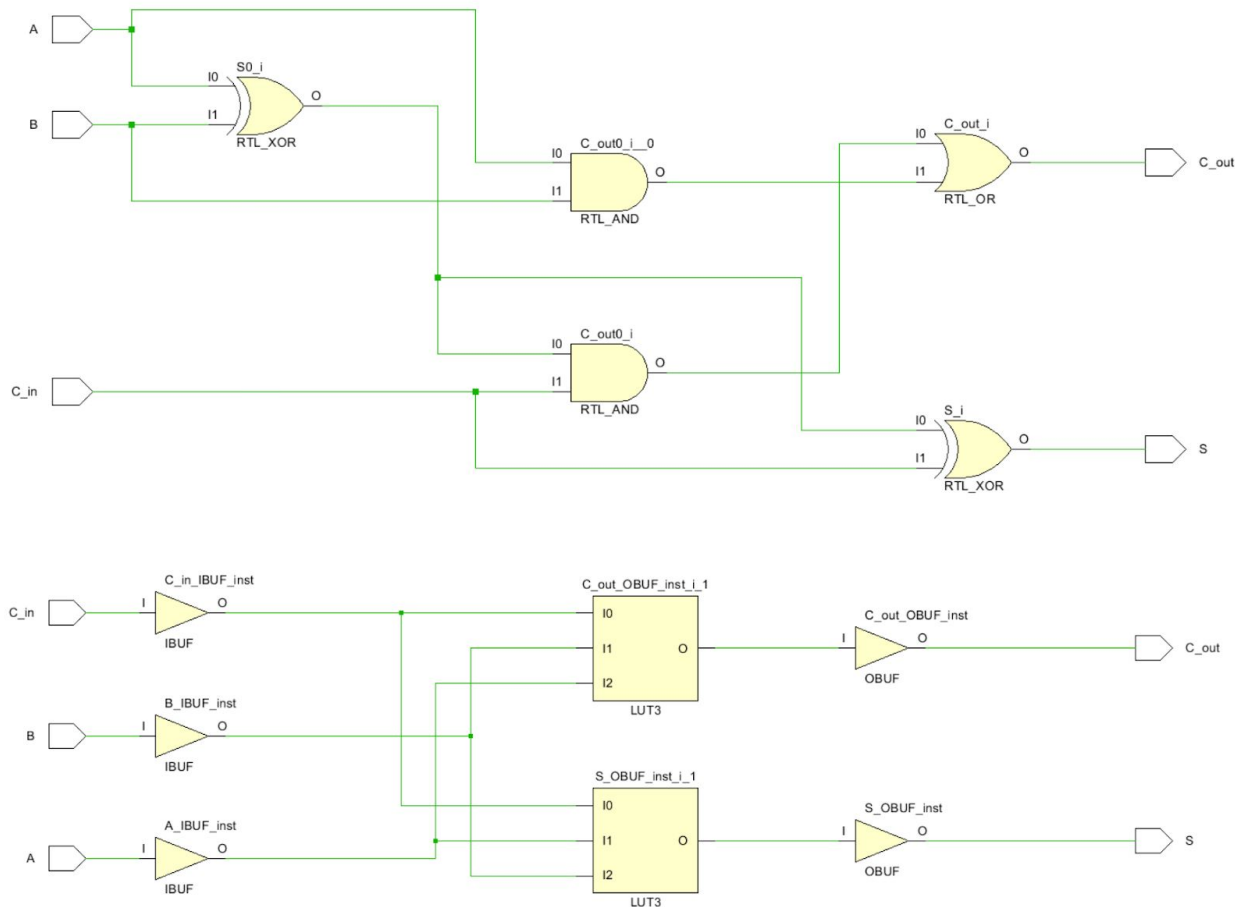

4-bit Ripple Carry Adder

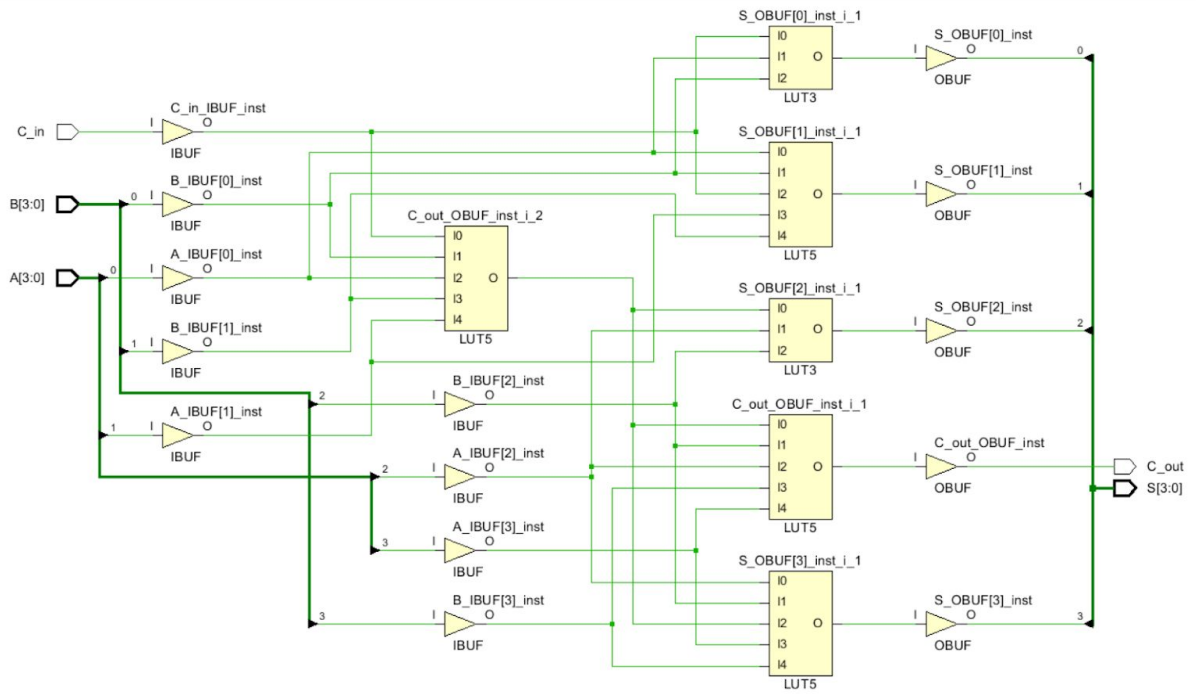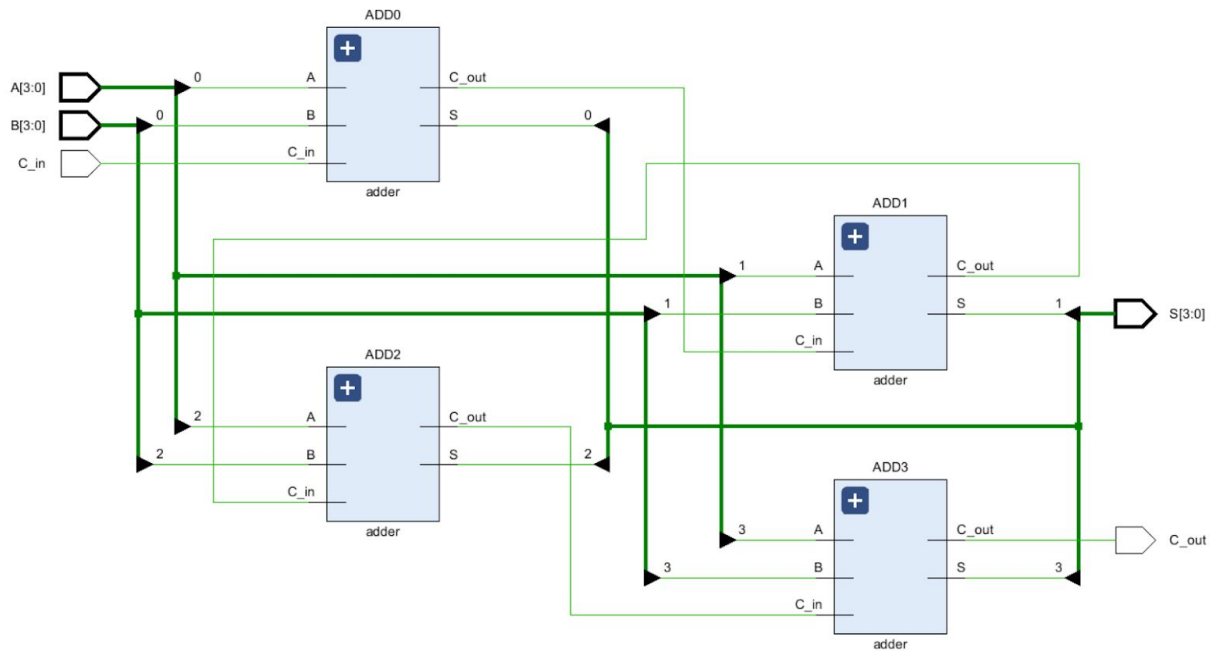

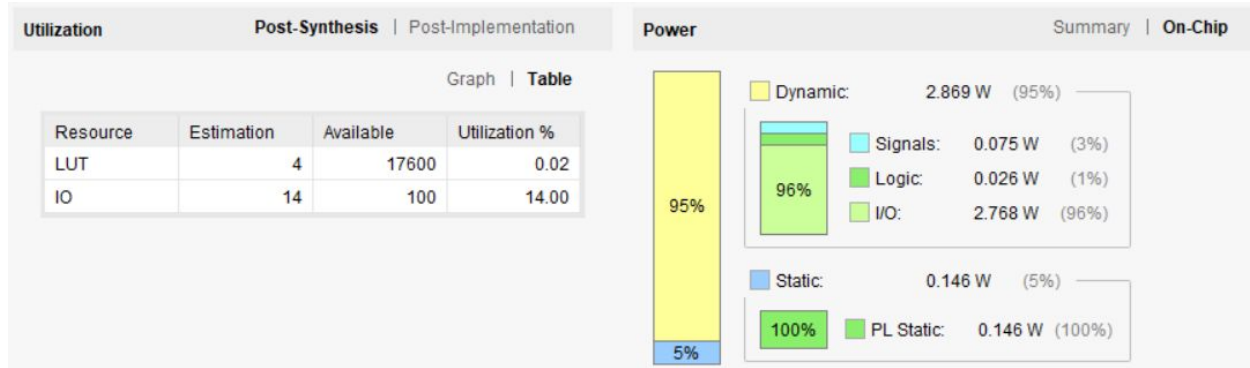

4. Part 2

a. Theory

A 16 function 4-bit ALU uses a 4-bit OPCODE to decide one of 15 possible arithmetic operations to implement. The operands A and B are 4-bits as well. The 4 switches on a Zybo board will set the value of the OPCODE, A, or B on the next rising edge of a clock when buttons 2, 1, or 0 are pressed respectively. The result of the operation is displayed on the 4 LEDs. Button 3 clears the values of OPCODE, A, and B and sets them to the default of "0000." The operations are

opcode	function	opcode	function
x"0"	$A + B$	x"8"	$A >>> 1$ (right shift arithmetic)
x"1"	$A - B$	x"9"	not A
x"2"	$A + 1$	x"A"	A and B
x"3"	$A - 1$	x"B"	A or B
x"4"	$0 - A$	x"C"	A xor B
x"5"	$A > B$ (greater than - see note)	x"D"	A xnor B
x"6"	$A << 1$ (left shift logical)	x"E"	A nand B
x"7"	$A >> 1$ (right shift logical)	x"F"	A nor B

b. Schematic

c. Design

my_alu.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
```

```
entity my_alu is
```

```

port( clk : in std_logic;
      A, B : in std_logic_vector(3 downto 0);
      Opcode : in std_logic_vector(3 downto 0);
      ALU_out : out std_logic_vector(3 downto 0));
end my_alu;

architecture my_alu_arch of my_alu is
    signal funct : std_logic_vector(3 downto 0) := "0000"; -- Intermediate signal for
    ALU_out
begin

    ALU_out <= funct; -- funct will hold values from alu operations

    ALU_proc: process(clk)
    begin
        if rising_edge(clk) then
            case (to_integer(unsigned(Opcode))) is
                when 0 => funct <= std_logic_vector(unsigned(A) + unsigned(B));
                when 1 => funct <= std_logic_vector(unsigned(A) - unsigned(B));
                -- Case 2: convert int +1 to length 4 unsigned then add/sub to unsigned A
                -- Then convert all to std_logic_vector before assigning to funct
                when 2 => funct <= std_logic_vector((unsigned(A) + to_unsigned(1,4)));
                when 3 => funct <= std_logic_vector((unsigned(A) - to_unsigned(1,4)));
                when 4 => funct <= std_logic_vector((to_unsigned(0,4) - unsigned(A)));
                when 5 =>
                    if (unsigned(A) > unsigned(B)) then
                        funct <= "0001";
                    else
                        funct <= (others => '0');
                    end if;
                when 6 => funct <= std_logic_vector(unsigned(A) sll 1);
                when 7 => funct <= std_logic_vector(unsigned(A) srl 1);
                when 8 =>
                    if (A(3) = '1') then
                        funct <= ('1' & std_logic_vector(unsigned(A(3 downto 1))));
                    else
                        funct <= std_logic_vector(unsigned(A) srl 1);
                    end if;
                when 9 => funct <= std_logic_vector(not unsigned(A));
                when 10 => funct <= std_logic_vector(unsigned(A) AND unsigned(B));
                when 11 => funct <= std_logic_vector(unsigned(A) OR unsigned(B));
                when 12 => funct <= std_logic_vector(unsigned(A) XOR unsigned(B));
                when 13 => funct <= std_logic_vector(unsigned(A) XNOR unsigned(B));
                when 14 => funct <= std_logic_vector(unsigned(A) NAND unsigned(B));
                when 15 => funct <= std_logic_vector(unsigned(A) NOR unsigned(B));
                when others => funct <= (others => '0');
            end case;
        end if;
    end process ALU_proc;
end my_alu_arch;

```

Debounce.vhd

```

library IEEE;

```

```

use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity debounce is
    port( clk, btn : in  std_logic;
          dbnc      : out std_logic);
end debounce;

architecture debounce_arch of debounce is
    signal count : std_logic_vector(2 downto 0) := (others => '0'); -- 3 bit counter signal
    signal shift : std_logic_vector(1 downto 0) := (others => '0'); -- 2 shift register

begin

    debounce: process(clk)
    begin
        if rising_edge(clk) then
            shift <= shift(0) & btn; -- Shift left 1, put btn at shift(0)

            if ((shift(1) = '1') AND (unsigned(count) /= 4)) then -- Check if shift(1) = 1 then
                check and increment counter
                count <= std_logic_vector(unsigned(count) + 1); -- Increment count when
                shift(0) = 1 and count < 4
            elsif ((shift(1) = '1') AND (unsigned(count) = 4)) then
                dbnc <= '1'; -- When count = 4, debounce output = 1. Now count and dbnc
                won't change until next shift(0) = 0
            else
                dbnc <= '0';
                count <= (others => '0'); -- Reset count if shift(0) = 0
            end if;
        end if;
    end process debounce;

end debounce_arch;

```

Alu_tester.vhd

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity alu_tester is
    port( clk      : in  std_logic;
          btn, sw   : in  std_logic_vector(3 downto 0);
          led       : out std_logic_vector(3 downto 0));
end alu_tester;

architecture alu_tester_arch of alu_tester is
    signal btn_val : std_logic_vector(3 downto 0) := "0000";
    signal A_val   : std_logic_vector(3 downto 0) := "0000";
    signal B_val   : std_logic_vector(3 downto 0) := "0000";
    signal Op_val  : std_logic_vector(3 downto 0) := "0000";

```

```

component my_alu
  port( clk : in std_logic;
        A, B : in std_logic_vector(3 downto 0);
        Opcode : in std_logic_vector(3 downto 0);
        ALU_out : out std_logic_vector(3 downto 0));
end component;

```

```

component debounce
  port( clk, btn : in std_logic;
        dbnc : out std_logic);
end component;

```

```

begin

```

```

alu_test_proc: process(clk)
begin
  if rising_edge(clk) then
    case (btn_val) is
      when "0001" => B_val <= sw;
      when "0010" => A_val <= sw;
      when "0100" => Op_val <= sw;
      when "1000" =>
        Op_val <= (others => '0');
        A_val <= (others => '0');
        B_val <= (others => '0');
      when others =>
        end case;
    end if;
  end process alu_test_proc;

```

```

-- 4 debounce circuits for 4 buttons

```

```

btn0: debounce
  Port Map(
    clk => clk,
    btn => btn(0),
    dbnc => btn_val(0)
  );

```

```

btn1: debounce
  Port Map(
    clk => clk,
    btn => btn(1),
    dbnc => btn_val(1)
  );

```

```

btn2: debounce
  Port Map(
    clk => clk,
    btn => btn(2),
    dbnc => btn_val(2)
  );

```

```

btn3: debounce

```

```

Port Map(
    clk => clk,
    btn => btn(3),
    dbnc => btn_val(3)
);

```


```



alu: my_alu
Port Map( clk => clk,
    A    => A_val,
    B    => B_val,
    Opcode => Op_val,
    ALU_out => led
);

```

end alu_tester_arch;

d. Implementation

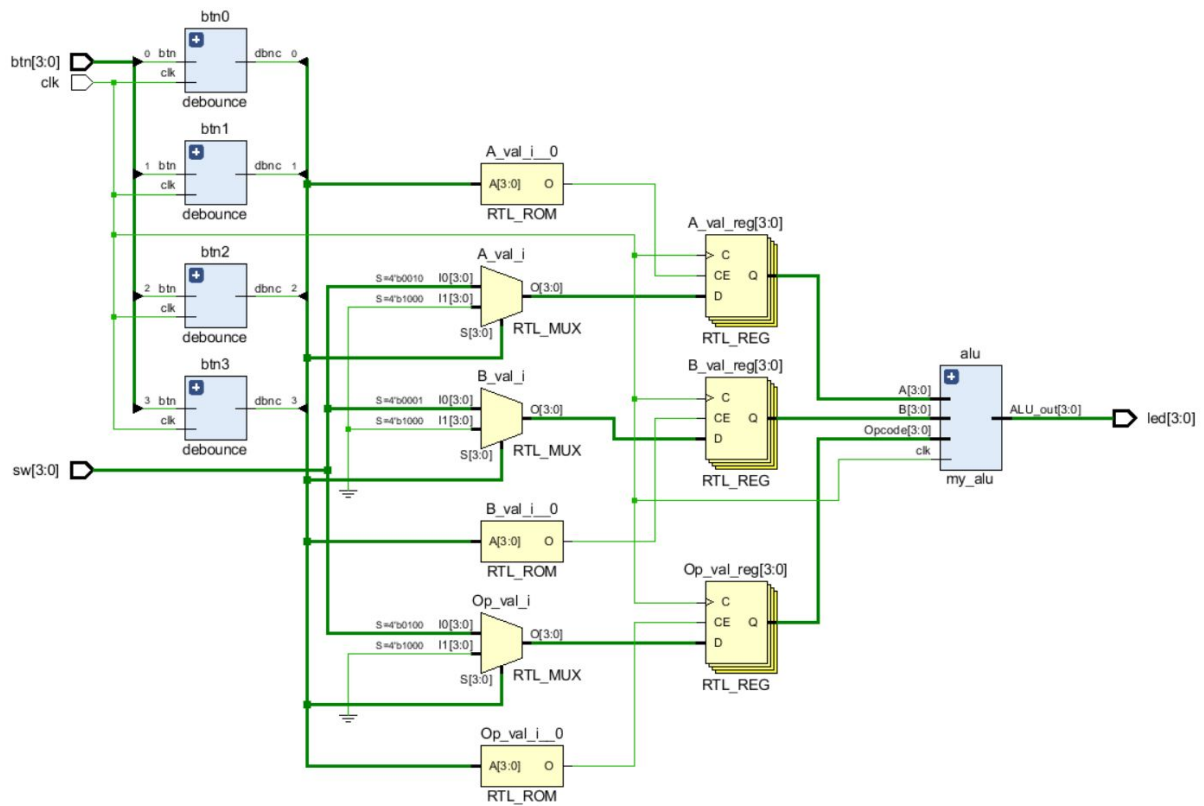

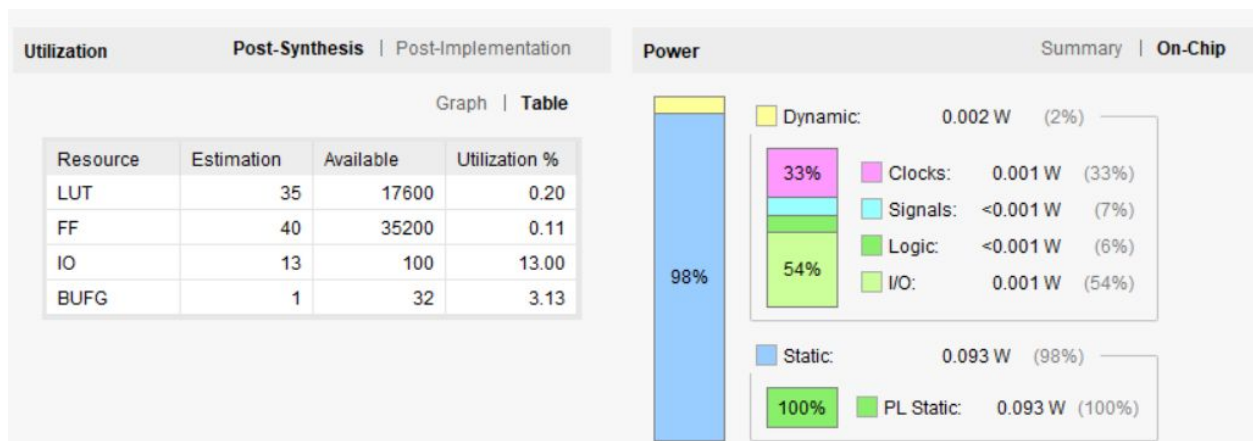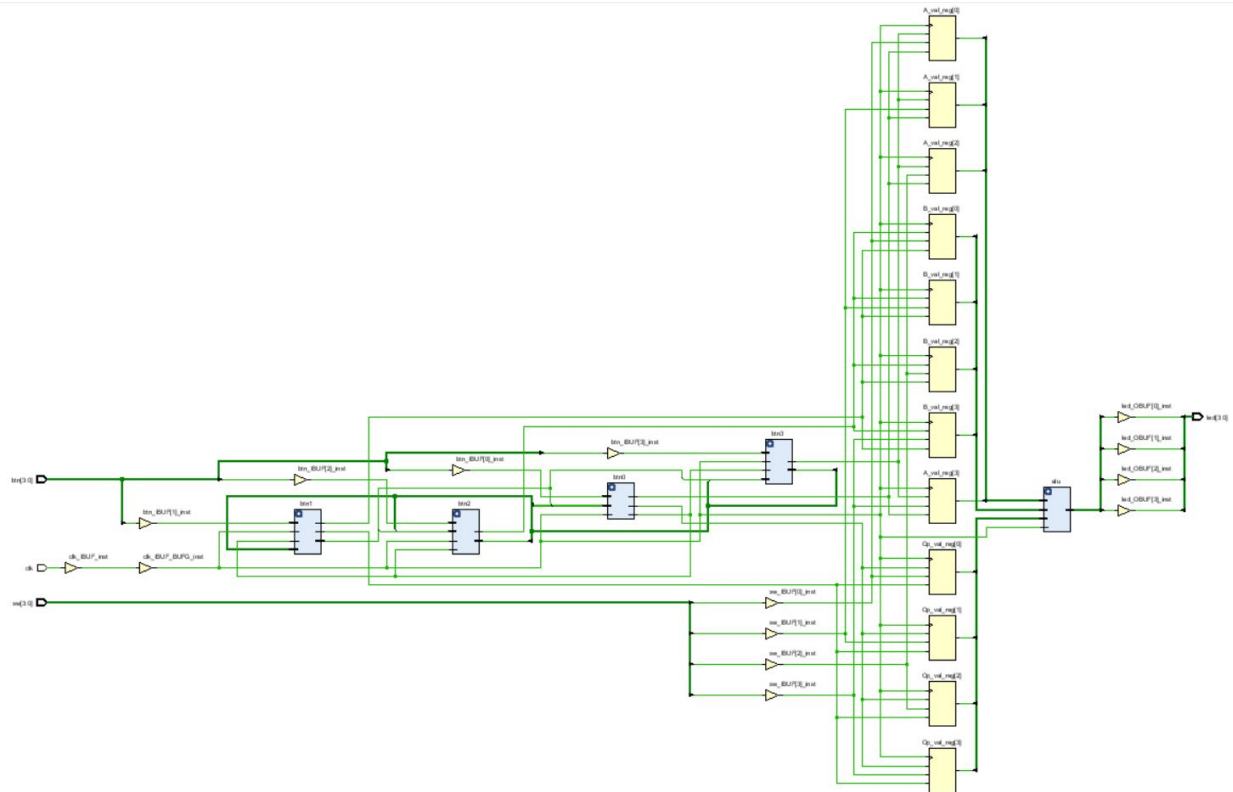

On Zybo_Master.xdc, I uncommented the lines for the clock, 4 LEDs, Switches, and Buttons so I can use them to assign values to A, B, C_{IN} and view the output of the ALU.



5. Discussion

a. Observation/Discoveries

The first part is just more practice with structural models for the first part. The adder isn't designed to be synchronous so concurrent assignments can be made

(data-flow model) for a single bit adder. Then the structural model is used to tie them together into a 4-bit ripple carry adder.

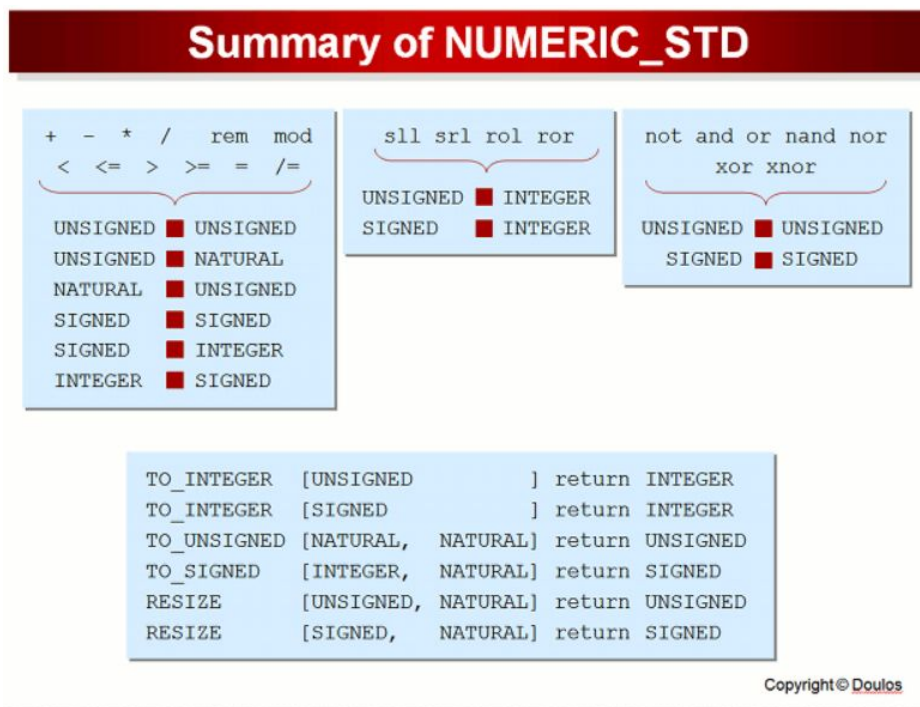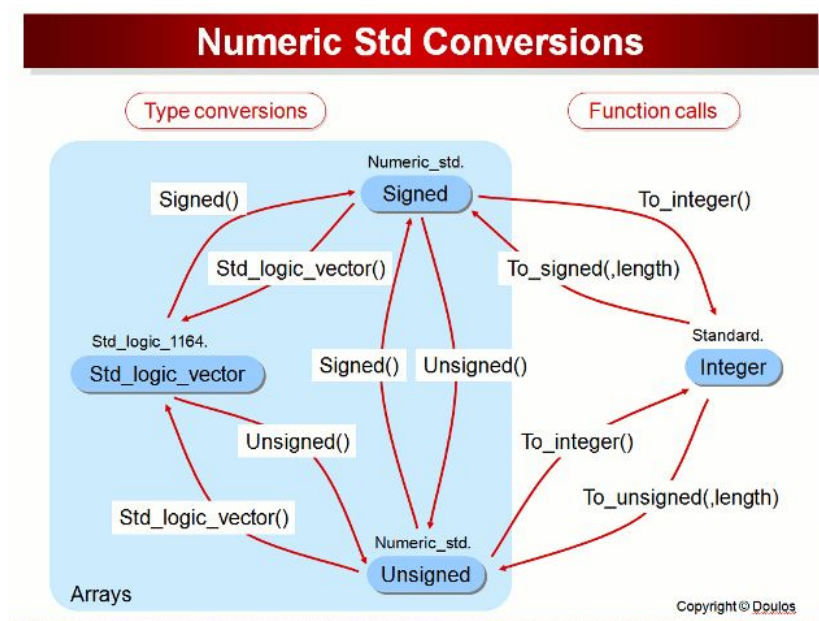For the ALU, a lot of data type casting has to be done using the numeric_std functions. Certain numeric_std operations can only be done between certain data types so we have to cast it into that type before performing any arithmetic.



I can also hover over signals and it would tell me the data type in Vivado. There was a situation with the buttons where I only had to do something in the cases “0001”, “0010”, “0100”, and “1000.” When using a case statement for them, although I wanted nothing to happen for any other button inputs, I had to put an “when others =>” line to get the code to work. I didn’t put any operations or assignments for that case and left it blank.

b. Questions/Follow Up

The first part is straightforward and I have no questions about logical operations and structural models. I also understand the need to cast data into different types. But I feel that keeping track of which signals are what type is tedious.